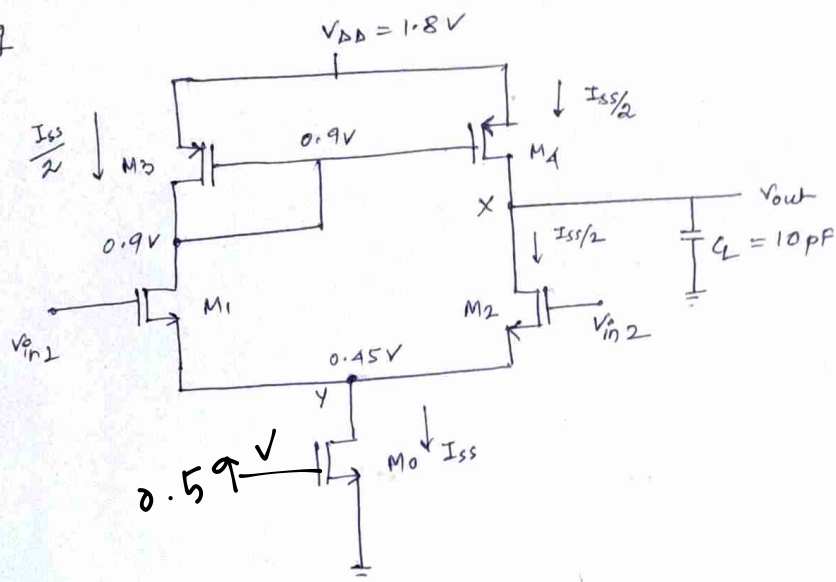


Differential Amp with Active load using PDM (potential Division Method).

Designing using
PDM




Specification: Technode \Rightarrow g_{pdk} 180nm $L = 500nm$ ($\approx 3 \times 180nm$)
 $A_v = 40dB$, $slewRate = 5V/\mu sec$, $Gain-BW = 5MHz$.

$$\# V_{out} = \frac{V_{DD}}{2} = 0.9 \quad \therefore V_Y = 0.45 \quad V_X = V_{out} = 0.9V_{th}$$

$$I_{SS} = SlewRate \times C_L$$

$$= 5V/\mu sec \times 10pF = 50\mu A. \quad \therefore \frac{I_{SS}}{2} = 25\mu A.$$

Transistor sizing.

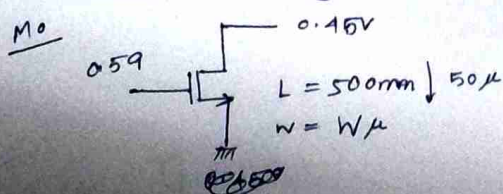


$$V_A = V_S + V_{th} + 5\%V_{DD}$$

$$= 0 + 500m + 90m = 590mV$$

vary $W \rightarrow 100n$ to 50μ

from I_D vs W @ $I_D = 50\mu A$ $W_0 = 10.04\mu$

M1

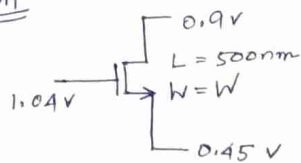

$$V_G = V_S + V_{th} + 5\% V_{DD}$$


$$= 450m + 590m = 1.04V$$

from I_D vs W at $I_D = 25\mu A$ $W_1 = 5.04\mu$

so, $W_1 = W_2 = 5.04\mu m$

PMOS


M3

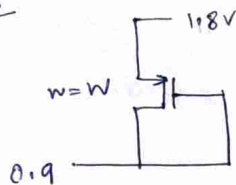

$$V_G = 0.9$$

from I_D vs W at $I_D = 25\mu A$ $W_3 = 2.285\mu$

$W_3 = W_4 = 2.285\mu$

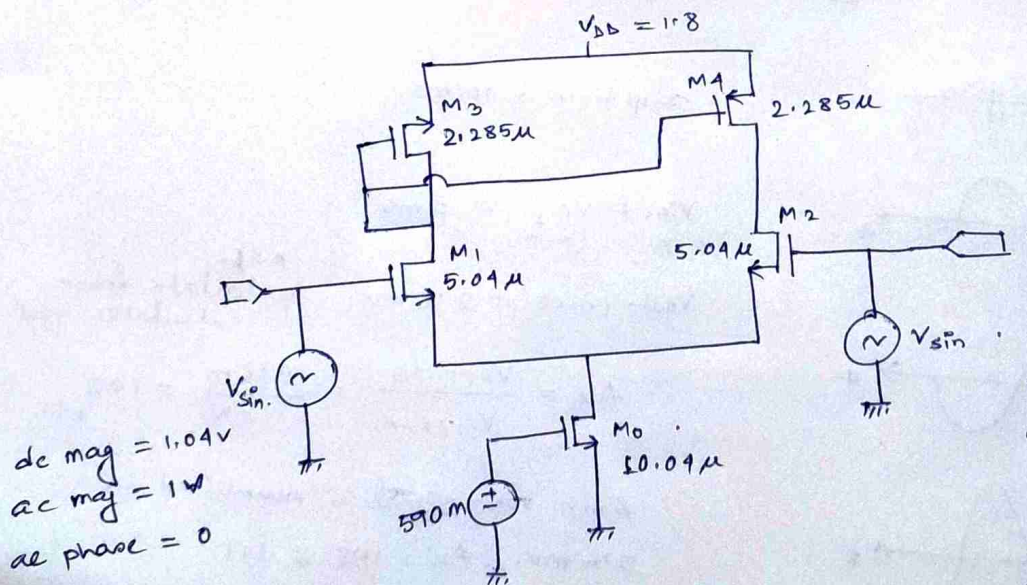

dc mag = 1.04v
ac mag = 1v
ac phase = 0

Amp = 1mV
freq = 1KHz.

Initial sinusoidal phase = 0

dc mag = 1.04v
ac mag = 1v
ac phase = 180
Amp = 1mV
freq = 1KHz.
Initial sinusoidal phase = 180°


Observation :

→ DC analysis.

Run dummy dc analysis to check where potential is dividing according to the PDM analysis.

2) AC ~~Transient~~ Analysis:

freq sweep 1 - 10 GHz.

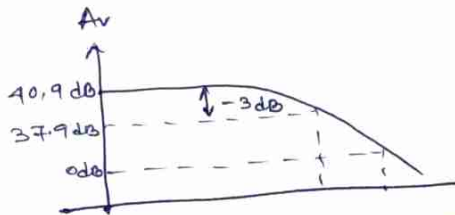

$$f_{3dB} = 111.379 \text{ KHz.}$$

$$f_{0dB} = 12.67 \text{ MHz.}$$

from plot

$$f_{3dB} = 111.379 \text{ KHz.}$$




$$f_{0dB} = 12.67 \text{ MHz.}$$

from plot

$$A_v(\text{dB}) = 10.9143 \approx 41$$

$$A_v(\text{Mag}) = 112 \cdot 1V$$

3) Transient - Analysis :

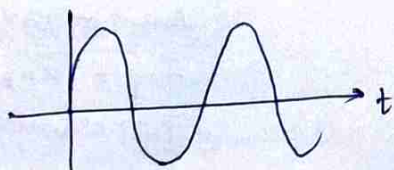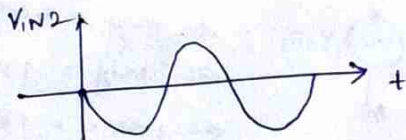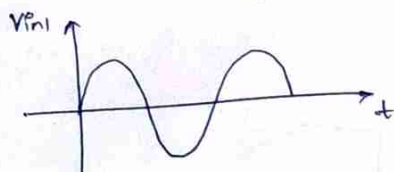

stop time = 10 ms.

$$V_{in1} \approx V_{in2} = 2 \text{ mV}$$

(P-P) (P-P)

$$V_{out}(\text{P-P}) = 216 \text{ mV}$$

ADD calculate from calculator tool


$$A_v = \frac{V_o(\text{P-P})}{V_{in}(\text{P-P})} = \frac{216 \text{ m}}{2 \text{ m}} = 108$$

2 mV volt signal is amplified to 216 mV. $A_v = 108 \approx 111$

4) Slew Rate :

Replace V_{sin} by V_{pulse} .



stop time = 10 ns.

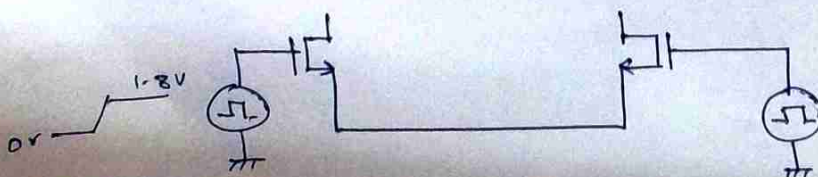

$V_1 = 0V$
 $V_2 = 1.8V$
 Period = 20 ns.
 pulse width = 10 ns

$V_1 = 1.8V$
 $V_2 = 0V$

period = 20 ns
 pulse width = 10 ns.

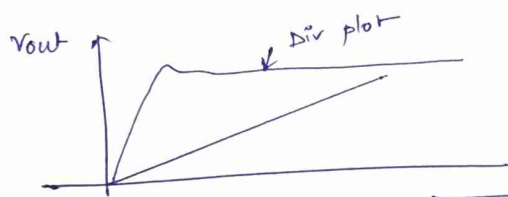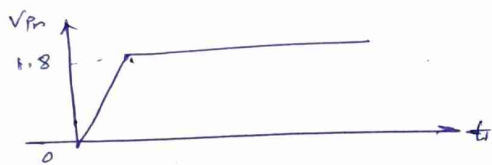

finding derivative using

from Dir plot \Rightarrow $\boxed{\text{Slew Rate} = 6.96 \text{ M} = 6.96 \text{ V}/\mu\text{sec}}$